

ME 3109: Measurement & Instrumentation



Azmir Hasan Mojumder
Lecturer

Department of Mechanical and Production Engineering
Ahsanullah University of Science and Technology


ME 3109: Measurement & Instrumentation

Topic_03: Analogue Signal Processing^[2]

1	Ideal Operational Amplifier (Op Amp)
2	Real Op Amp
3	Practical Example

[2] Histan, *“Introduction to Mechatronics & Measurement Systems”*, 4th Edition

1. Ideal Op Amp: Op Amp Jungle

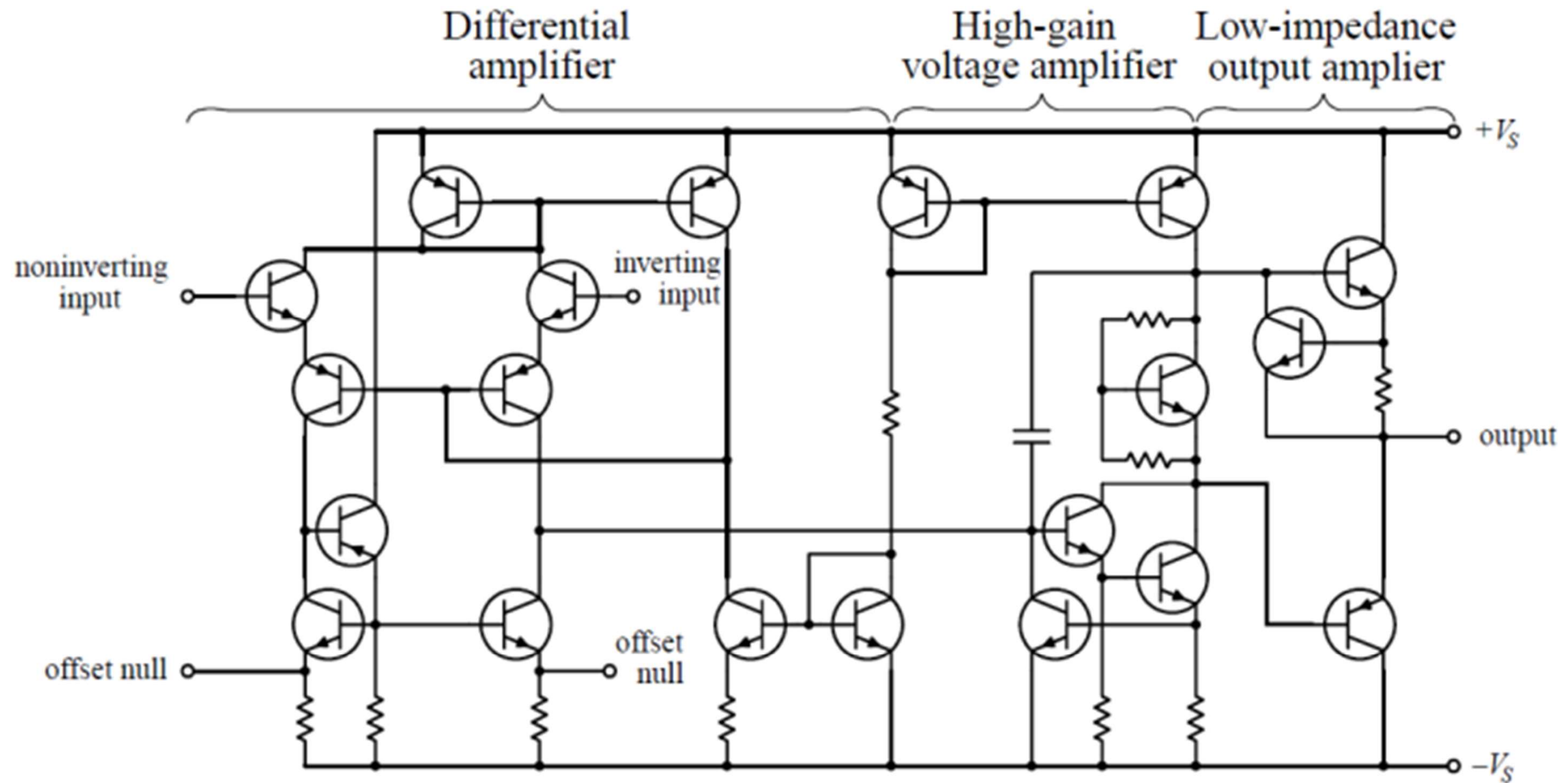

1. Ideal Op Amp


Reasons for Selecting Op Amp:



- ✓ Transducer converts physical quantities into analogue voltage or current
- ✓ These Signals are often too small, noisy, possess DC offset
- ✓ Op Amp is used to process these analogue signals
- ✓ Op Amp is an IC and active device; usually require $\pm 15\text{ V}$
- ✓ Building block of many important circuits such as Amplifiers; Integrator; Differentiator; Summer; Comparator; A/D and D/A converter; Active filter; Sample and Hold circuit etc.
- ✓ Op Amp are very easy to work with
- ✓ High input impedance and low output impedance
- ✓ Don't connect to power supply incorrectly! Might blow up

1. Ideal Op Amp

Ideal Model of Op Amp:

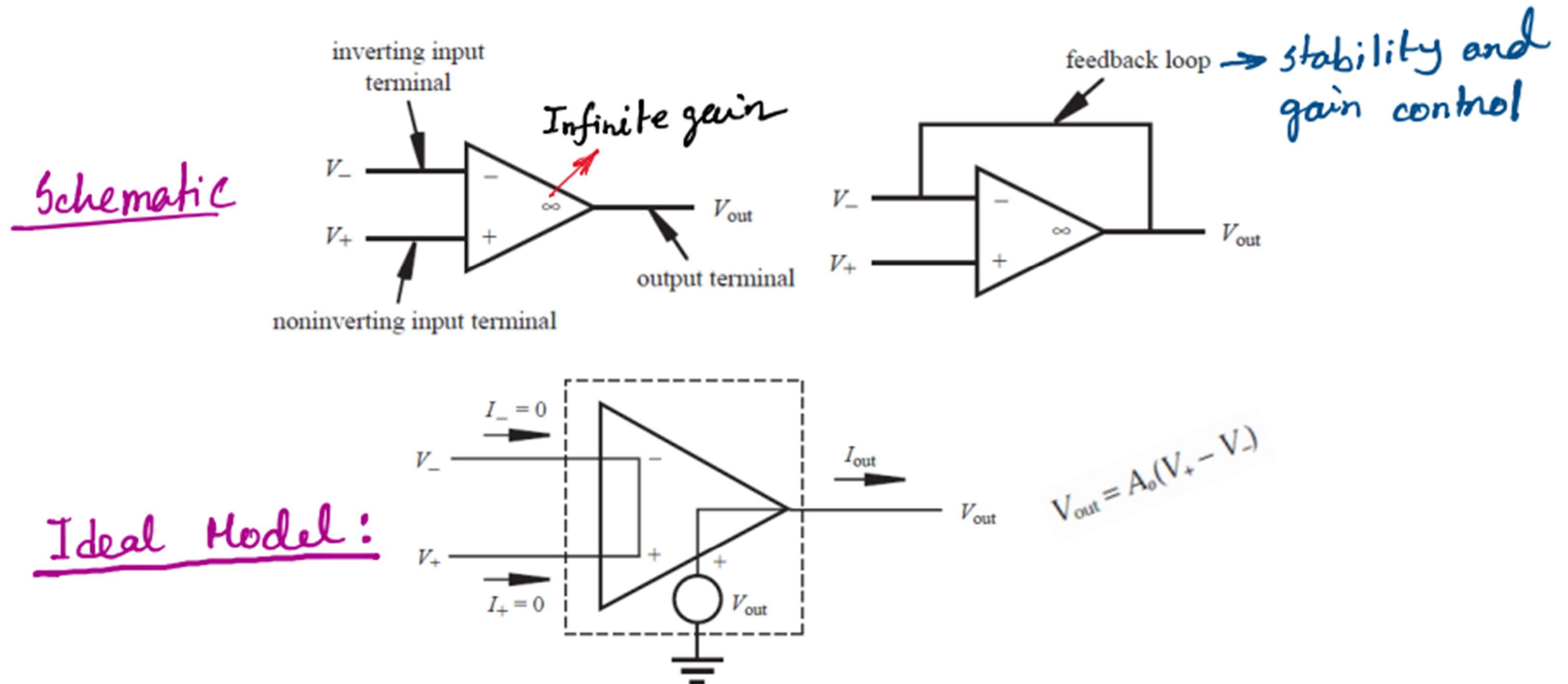

1. Ideal Op Amp

Op Amp Assumptions:


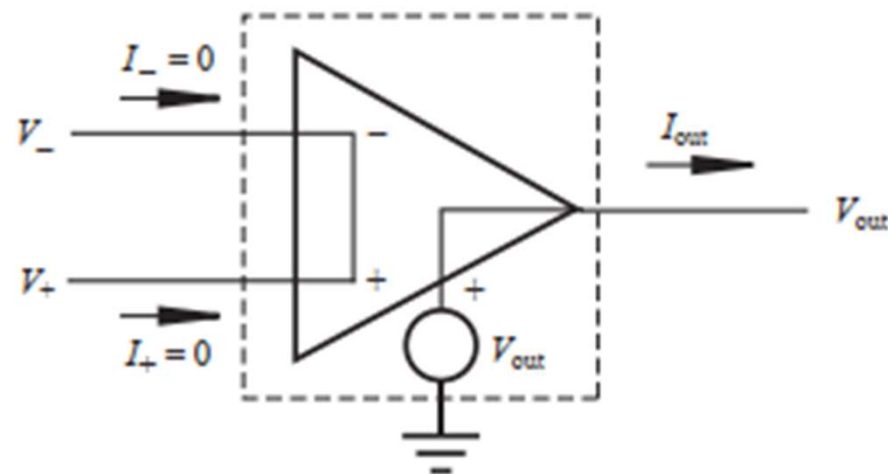


Figure 5.4 Op amp equivalent circuit.

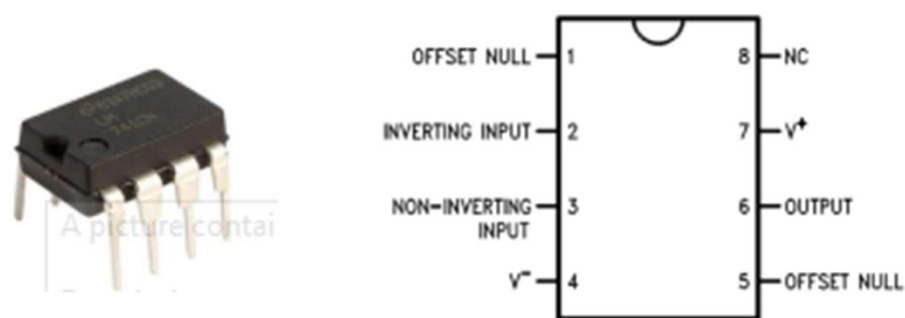

LH 741

1. *It has infinite impedance at both inputs; hence, no current is drawn from the input circuits. Therefore,*

$$I_+ = I_- = 0 \quad (5.4)$$

2. *It has infinite gain. As a consequence, the difference between the input voltages must be 0; otherwise, the output would be infinite. This is denoted in Figure 5.4 by the shorting of the two inputs. Therefore,*

$$V_+ = V_- \quad (5.5)$$


Even though we indicate a short between the two inputs, we assume no current may flow through this short.

3. *It has zero output impedance. Therefore, the output voltage does not depend on the output current.*

* This "illogical" ideal Op Amp provides close approximation of real op Amp.

1. Ideal Op Amp

Inverting Amplifier:

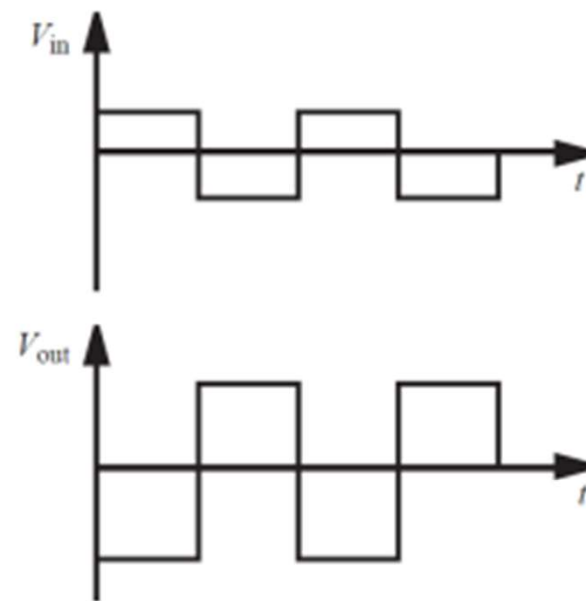

→ 180° phase-shift for periodic signal

node C, $i_{in} = -i_{out}$ and $V_c = 0$

∴ $V_{in} - V_c = i_{in} R \Rightarrow \underline{V_{in} = i_{in} R}$


nd, $V_{out} - V_c = i_{out} R_F \Rightarrow V_{out} = i_{out} R_F$

So, $V_{out} = -i_{in} R_F$

$\frac{V_{out}}{V_{in}} = -\left(\frac{R_F}{R}\right) \rightarrow \text{Voltage Gain}$

1. Ideal Op Amp


Non-inverting Amplifier:

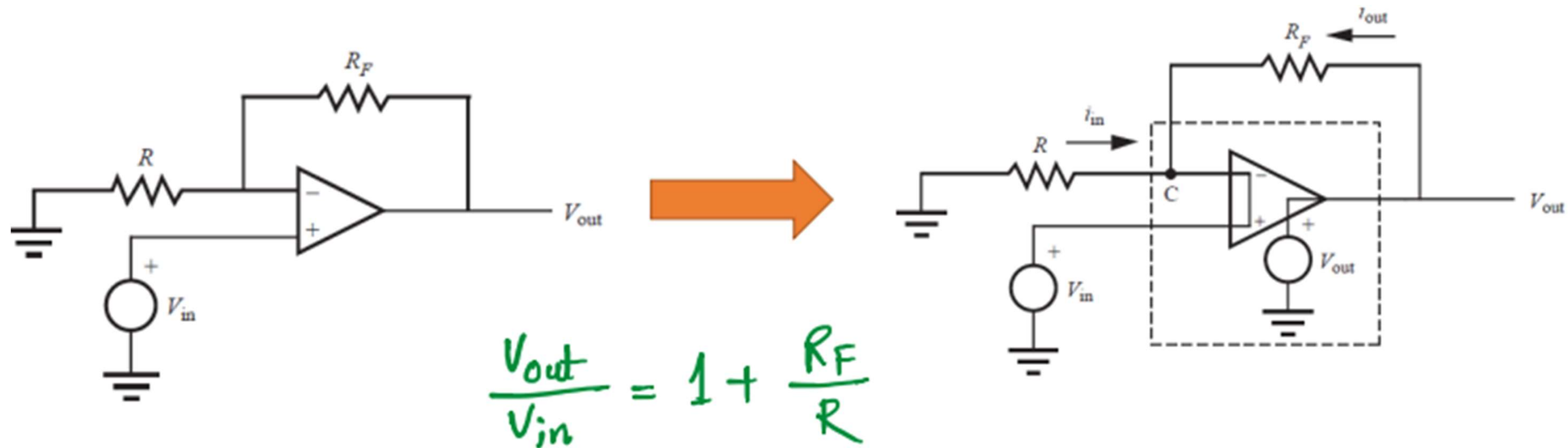

- ✓ Positive gain greater than or equal to 1 (Don't forget get low of thermodynamics)!!
- ✓ Useful in isolating one portion of a circuit from another

1. Ideal Op Amp

Buffer or Follower:

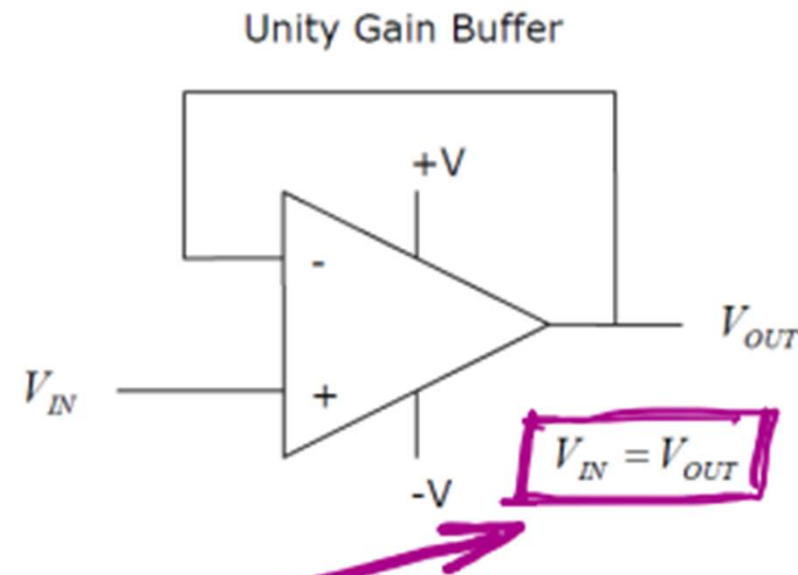


- ✓ $R_F=0$ and $R=\infty$
- ✓ It has a high input impedance and low output impedance
- ✓ This circuit is useful in applications where you need to couple to a voltage signal without loading the source of the voltage

→ source isolation from rest of the circuit

1. Ideal Op Amp

Summer:

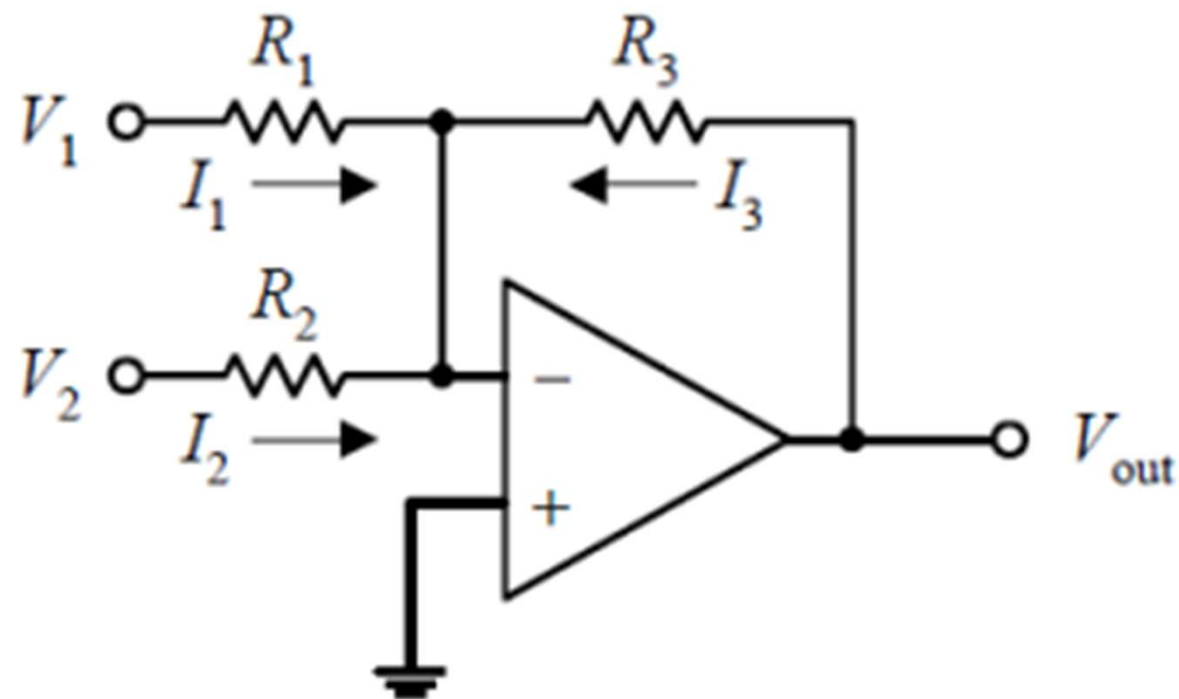


$$V_{out} = -\frac{R_3}{R_1} V_1 - \frac{R_3}{R_2} V_2 = -\left(\frac{R_3}{R_1} V_1 + \frac{R_3}{R_2} V_2\right)$$

Let, $R_1 = R_2 = R_3$

$V_{out} = -(V_1 + V_2)$

1. Ideal Op Amp


Summer:

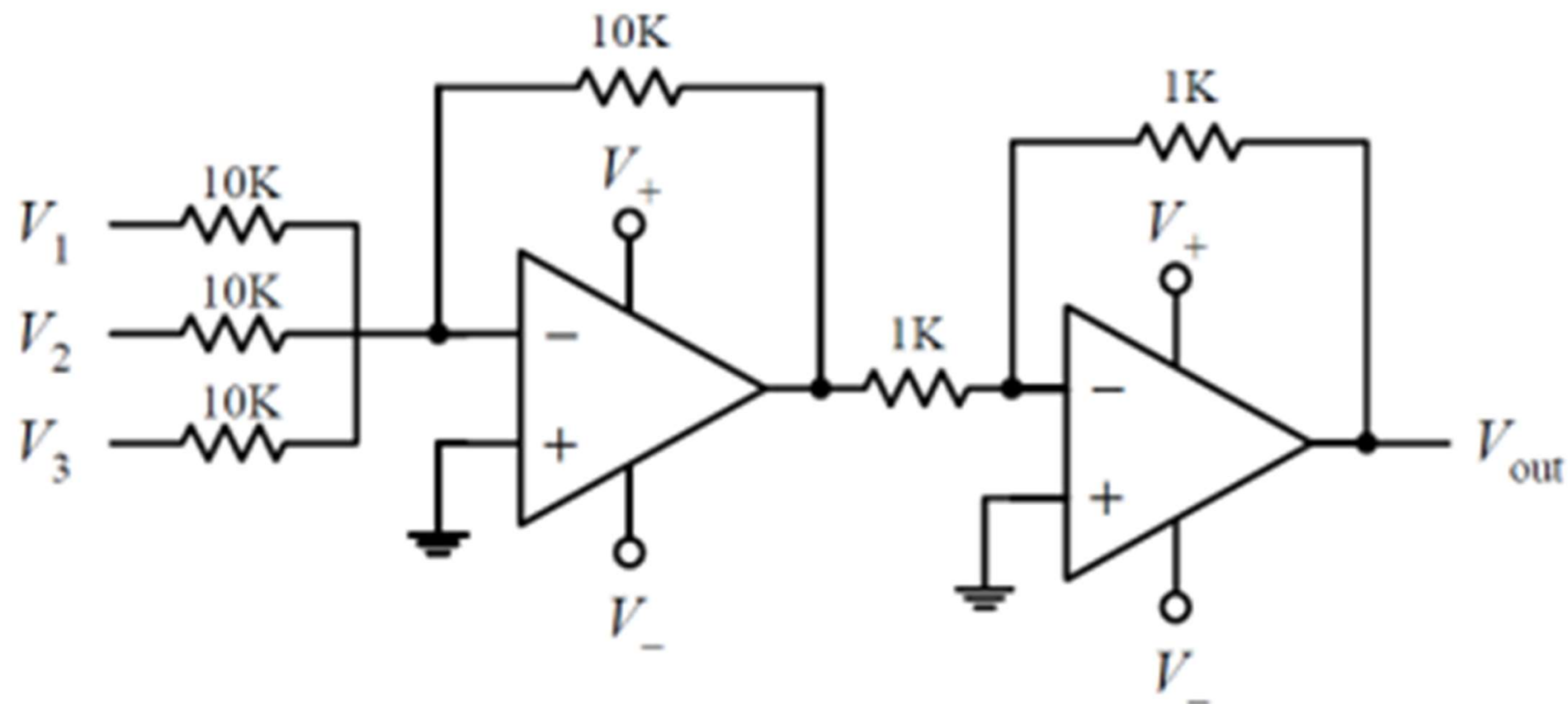


$V_{out} = ?$

1. Ideal Op Amp

Difference Amplifier:

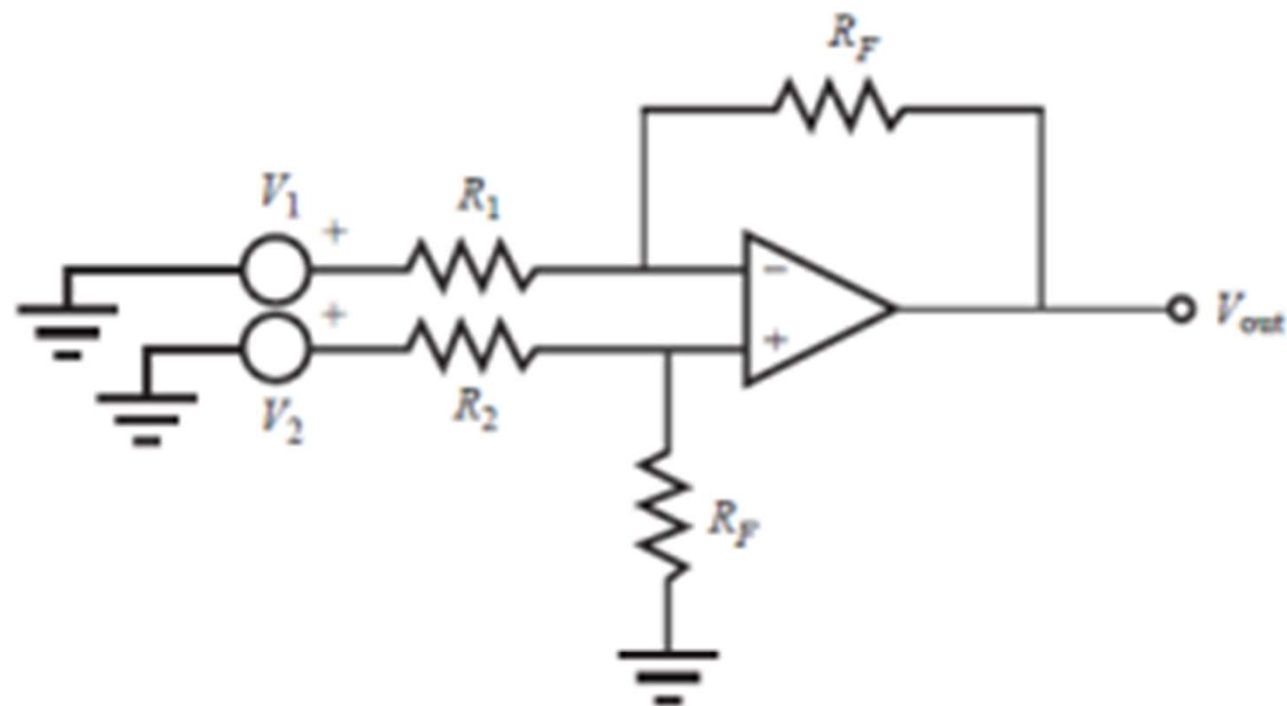

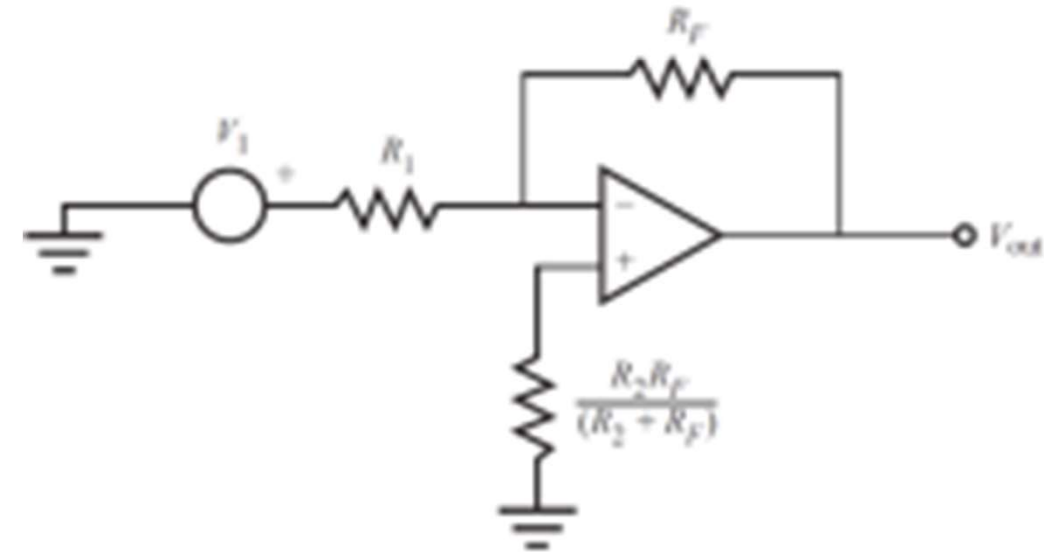
Principle of Superposition; $V_{out} \approx V_{out 1} + V_{out 2}$
1st, V_2 shorted, R_2 Grounded




$$\Rightarrow V_{out 1} = -\frac{R_F}{R_1} V_1$$

1. Ideal Op Amp

Difference Amplifier:

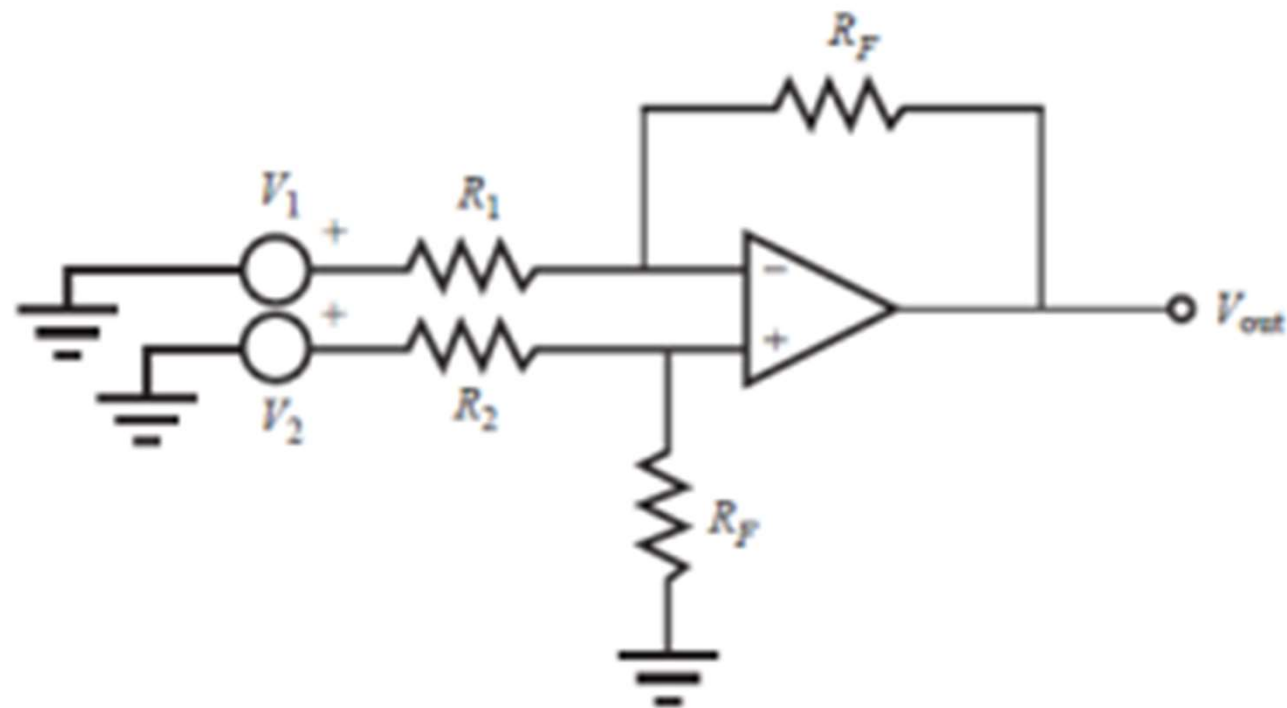

2nd, V_1 shorted and R_1 grounded

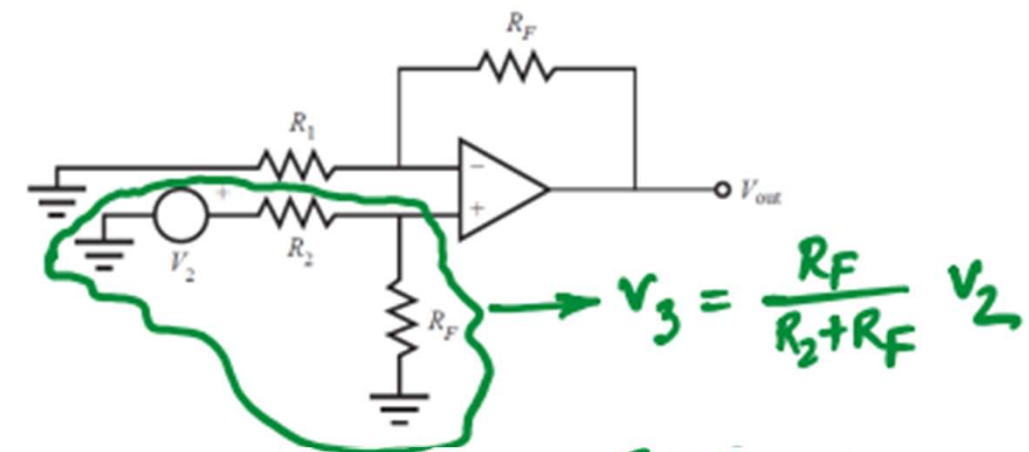

$$\Rightarrow V_{out2} = \left(1 + \frac{R_F}{R_1}\right) V_3$$

$$\therefore V_{out2} = \left(1 + \frac{R_F}{R_1}\right) \left(\frac{R_F}{R_2 + R_F}\right) V_2$$

If, $R_1 = R_2 = R$

$$V_{out} = \frac{R_F}{R} (V_2 - V_1)$$


1. Ideal Op Amp

Instrumentation Amplifier:

- ✓ Large Common Mode Rejection Ratio (CMRR). Ideal amplifier CMRR is infinite.

$\rightarrow \frac{\text{Difference Mode Gain}}{\text{Common Mode Gain}} \rightarrow \text{Amplification of average of } V_{in}s$



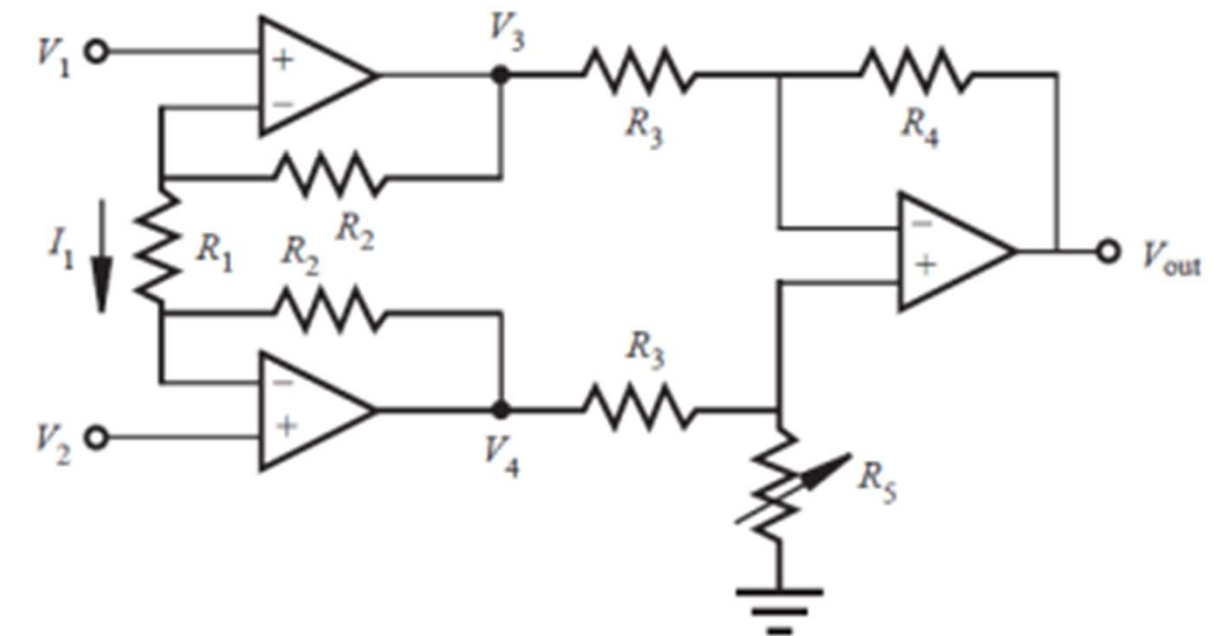
- ✓ Very high input impedance
- ✓ Low-level signals in a noisy environment
- ✓ Consistent bandwidth over a large range of gains
- ✓ A single external resistor is used to set the gain.
- ✓ This gain can be higher and more stable



for Max. CMRR, $R_4 = R_5 \rightarrow V_{out} = \left[\frac{R_4}{R_3} \left(1 + 2 \frac{R_2}{R_1} \right) \right] (V_2 - V_1)$


1. Ideal Op Amp

Integrator:

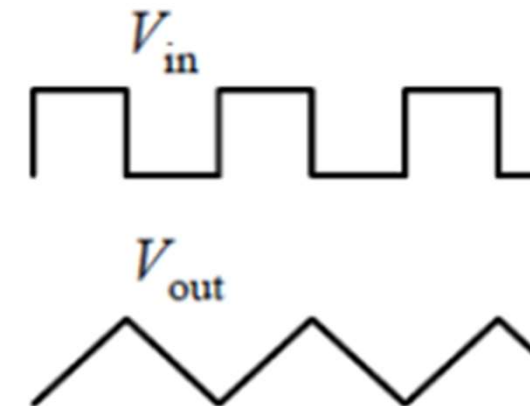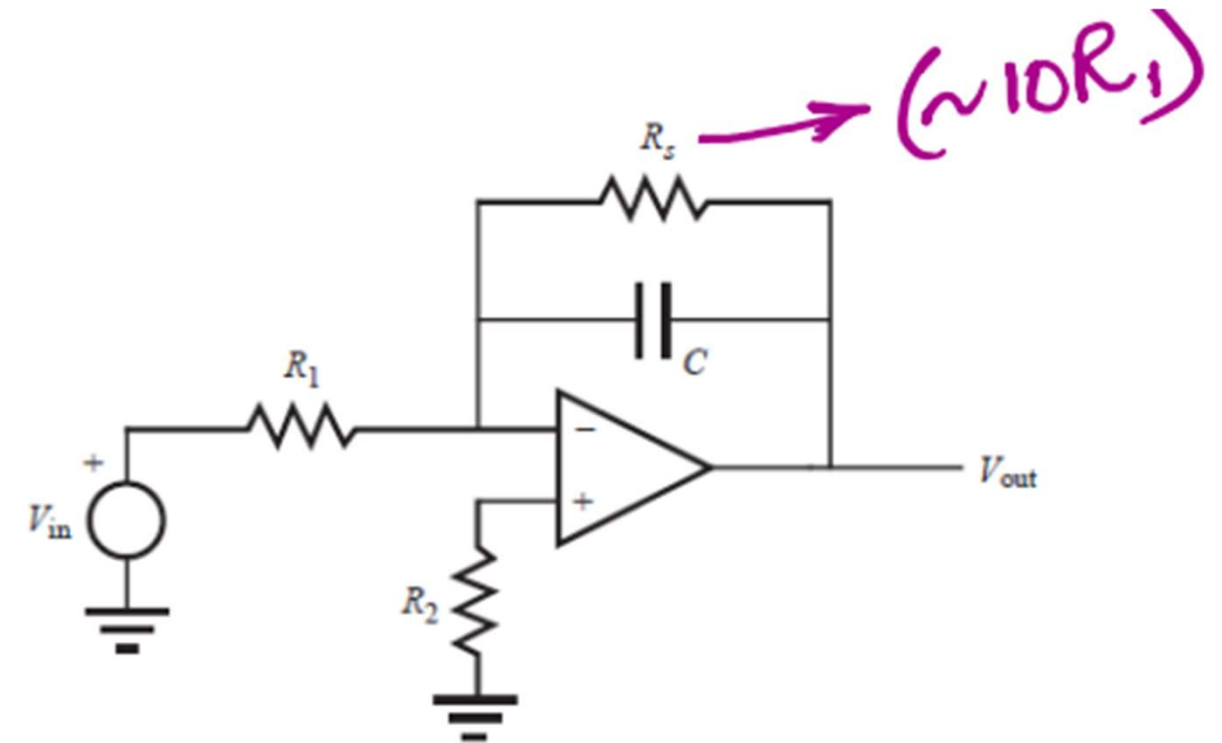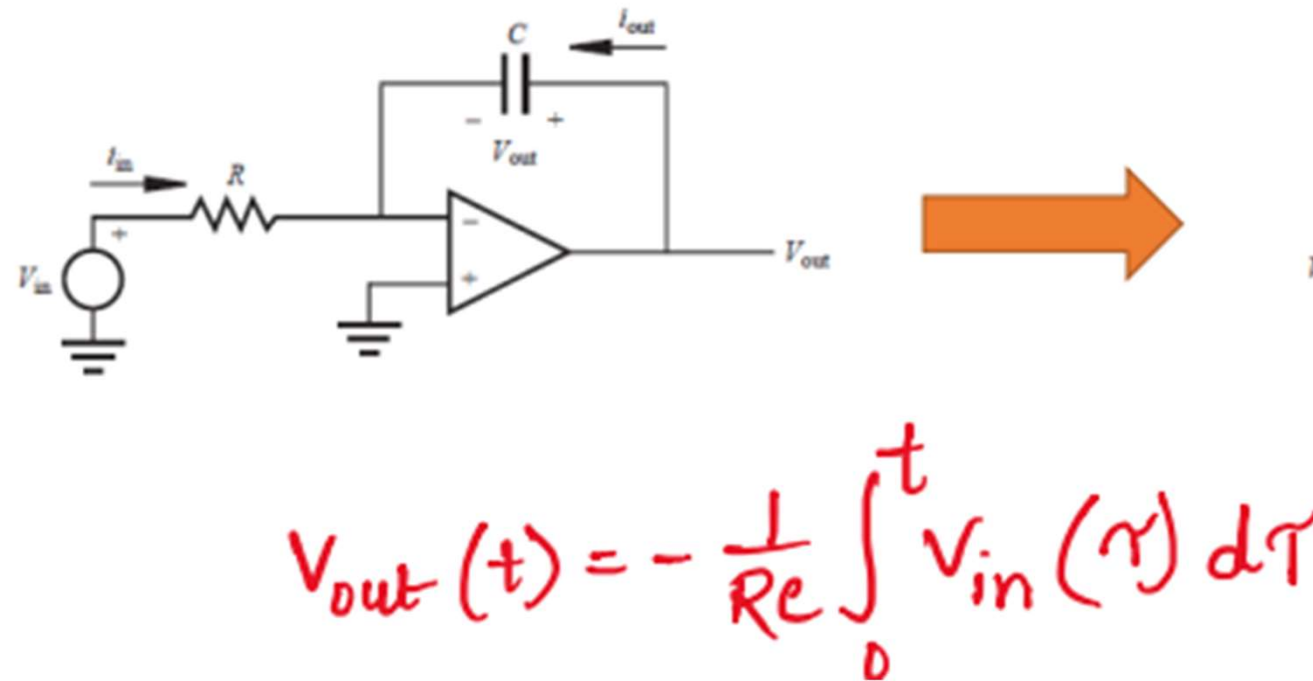

1. Ideal Op Amp

Integrator:

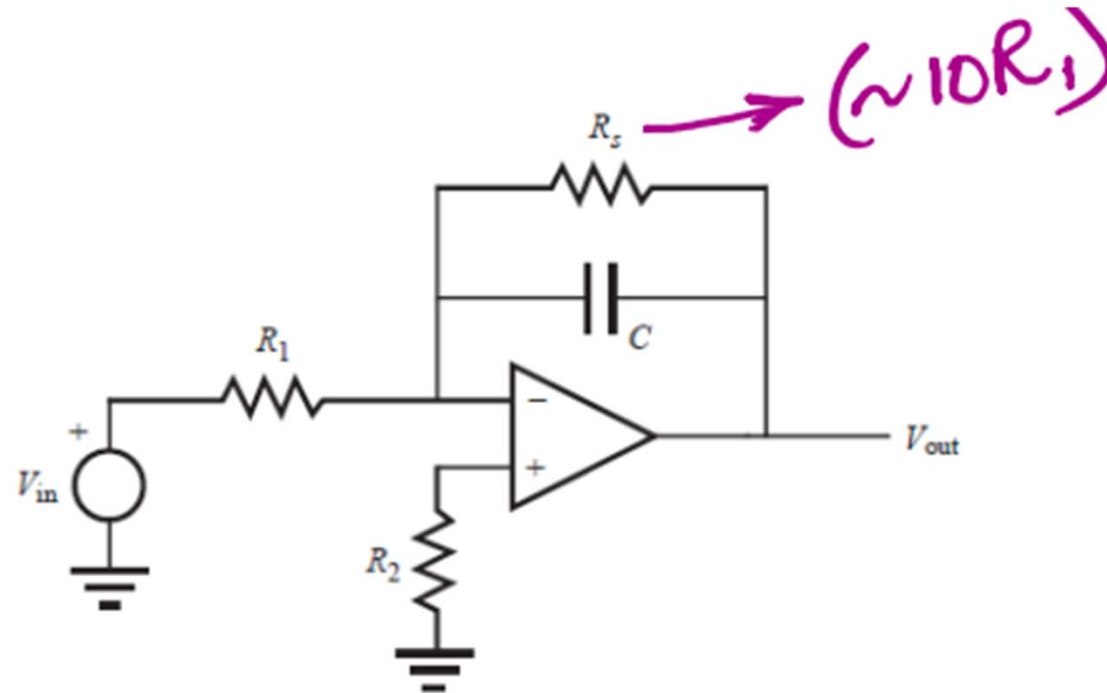


- ✓ The resistor R_s placed across the feedback capacitor is called a shunt resistor whose purpose is to limit the low-frequency gain of the circuit
- ✓ The circuit on the right acts as an integrator only for a range of frequencies
- ✓ Any DC offset due to the input bias current is minimized by R_2

$$\rightarrow \frac{R_1 R_s}{R_1 + R_s}$$

1. Ideal Op Amp

Differentiator:

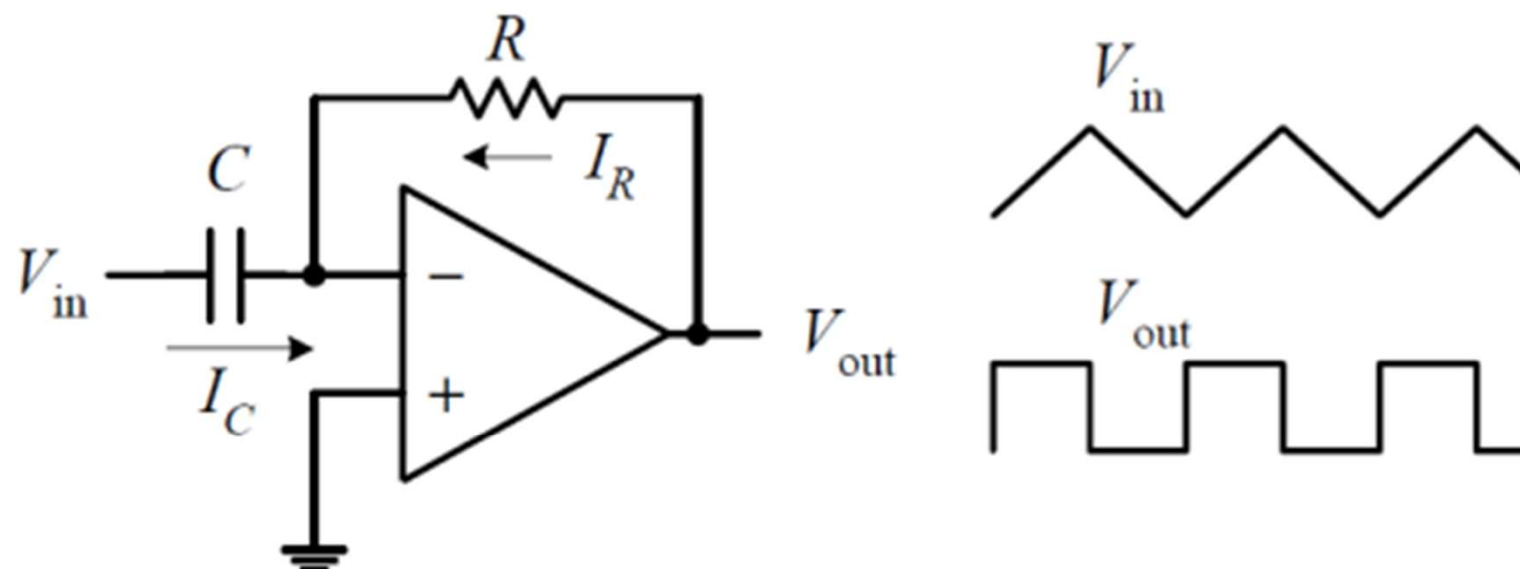

$$I_C = C \frac{dV}{dt} = C \frac{d(V_{in} - V_-)}{dt} = C \frac{d(V_{in} - 0V)}{dt} = C \frac{dV_{in}}{dt}$$


$$I_R = \frac{V_{out} - V_-}{R} = \frac{V_{out} - 0V}{R} = \frac{V_{out}}{R}$$

$$I_R + I_C = 0$$

$$V_{out} = -RC \frac{dV_{in}}{dt}$$

1. Ideal Op Amp

Differentiator:

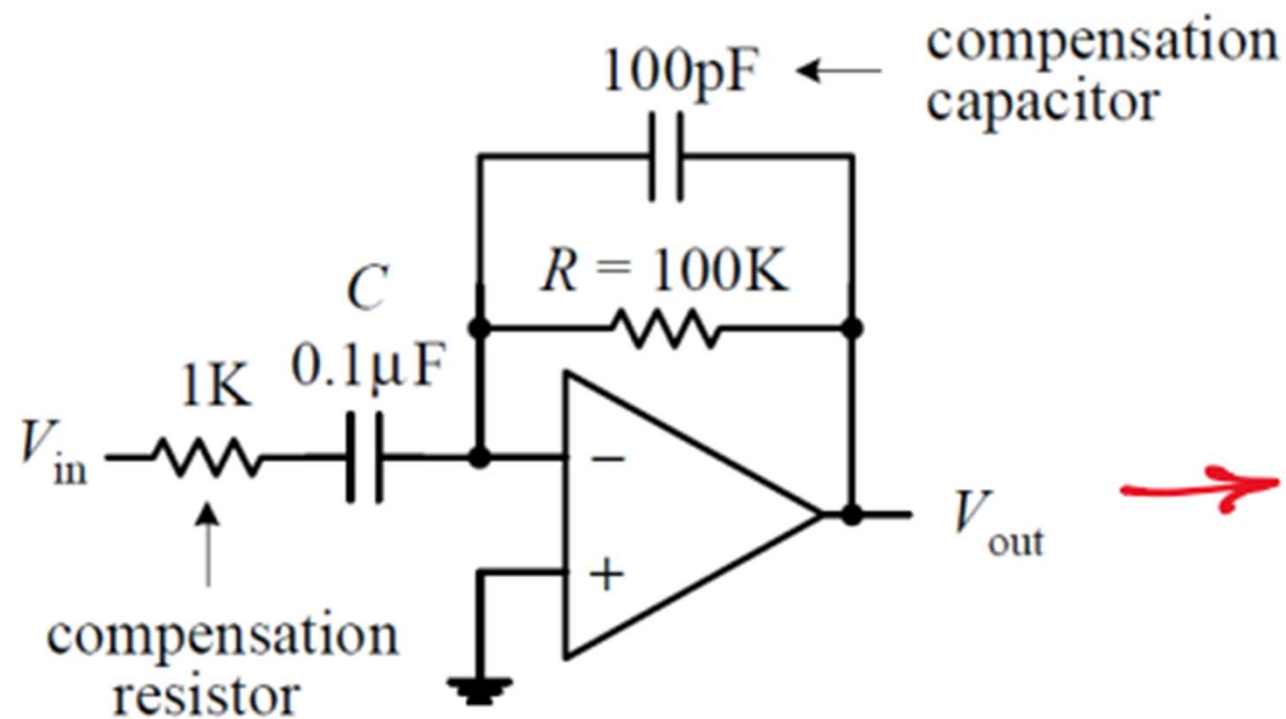


- Improved design
- Fast changing noise $\rightarrow V_{out} \uparrow\uparrow$
- Compensation capacitor & Resistor

An additional input-bias compensation resistor placed between the noninverting input and ground may be needed to avoid offset error caused by input bias current

1. Ideal Op Amp


Comparator:

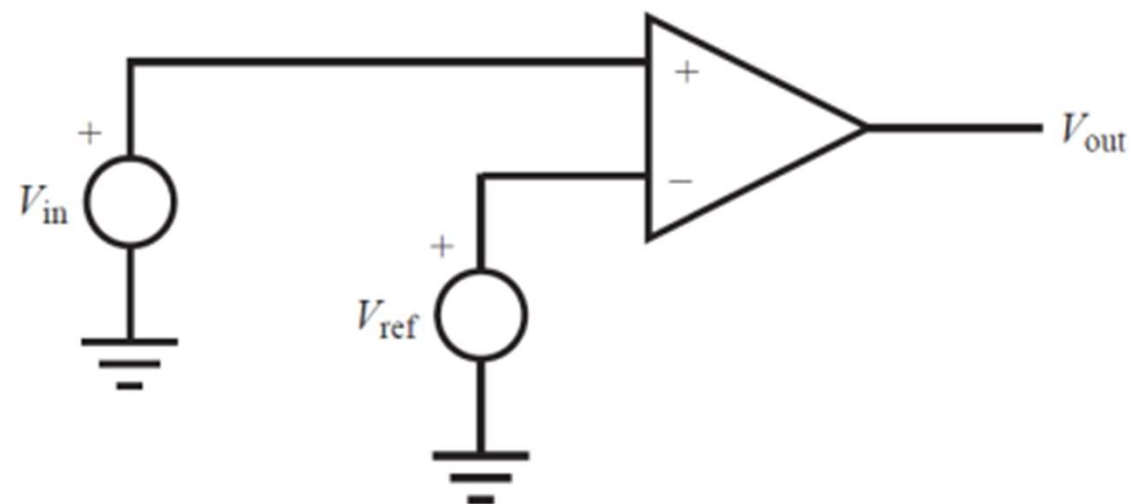

$$V_{out} = \begin{cases} +V_{sat} & V_{in} > V_{ref} \\ -V_{sat} & V_{in} < V_{ref} \end{cases}$$

1. Ideal Op Amp

Sample and Hold Circuit:

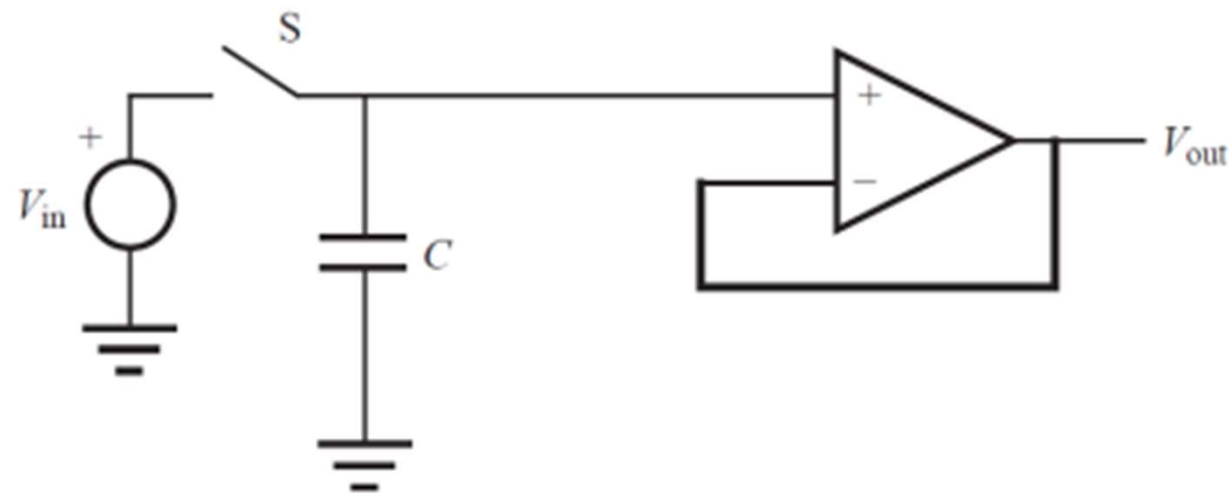


- ✓ Used extensively in analog-to-digital (ADC) conversion to stabilize the signal during conversion
- ✓ Low leakage capacitor is a good choice

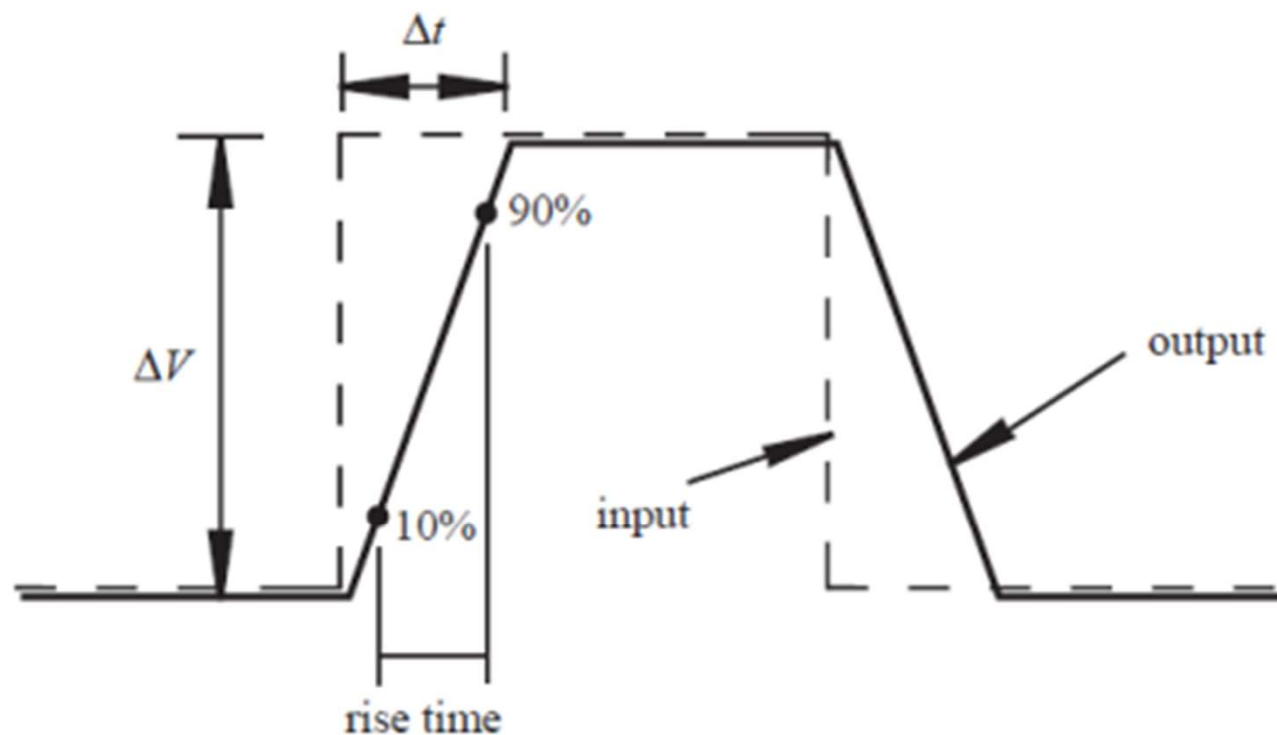2. Real Op Amp

Two important characteristics of a real op amp are associated with its response to a square wave input:

- Slew rate $\rightarrow \frac{\Delta V}{\Delta t}$
- Rise time



Consult data sheet for:

Input Resistance


Max. Output Voltage

Gain-Bandwidth Product (GBP)


CMRR

etc.

2. Real Op Amp

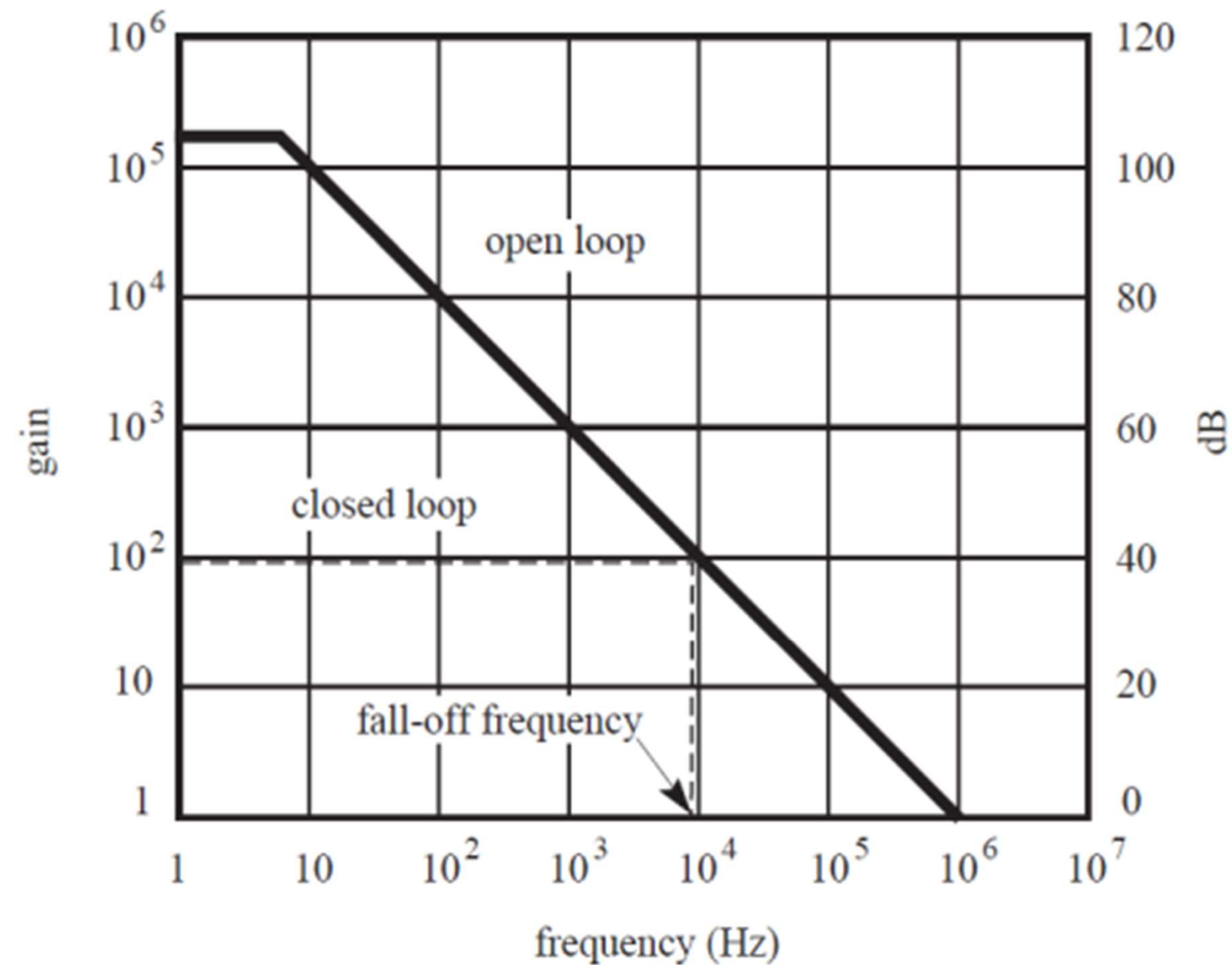


3. Practical Example

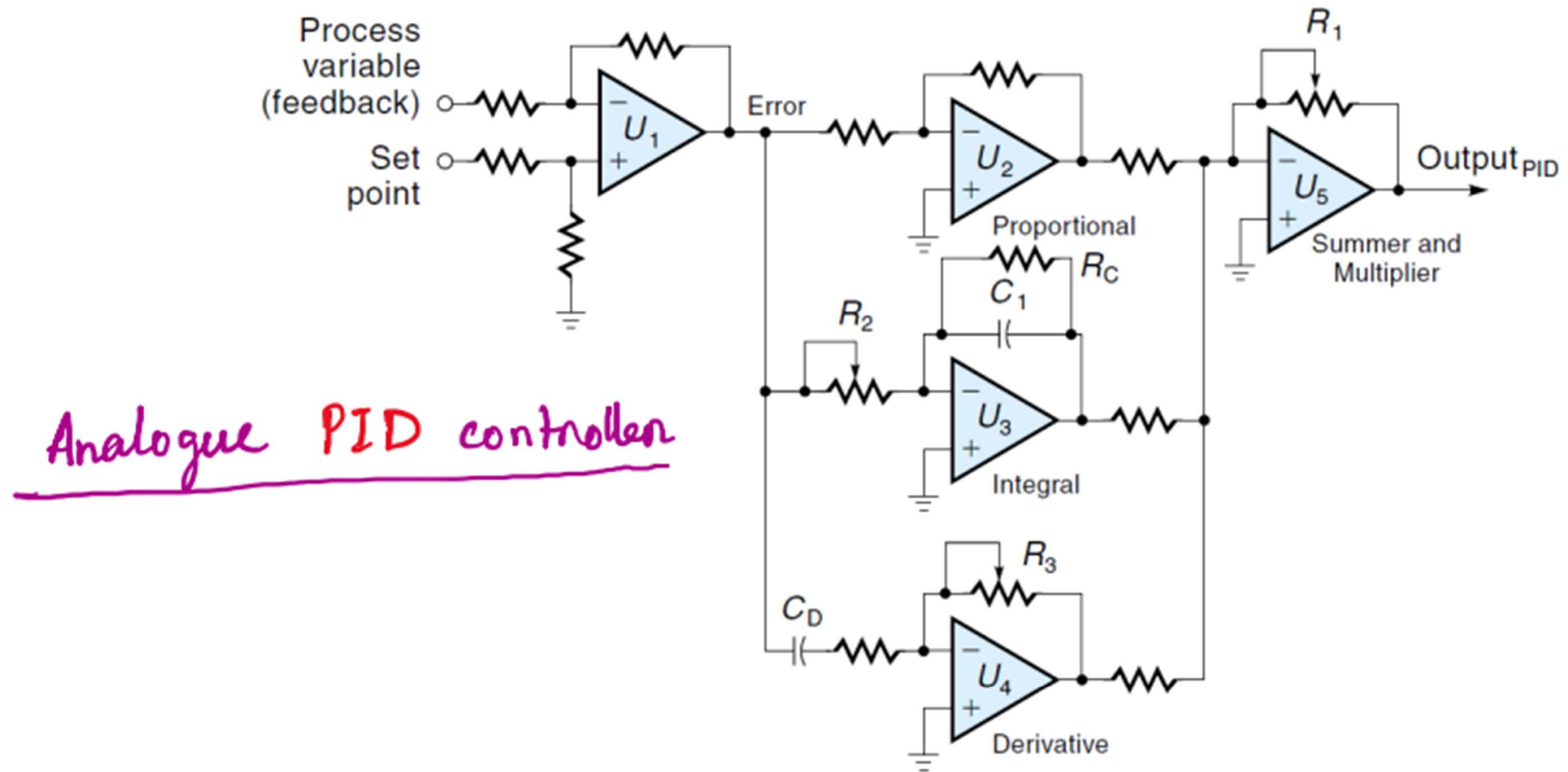


Kilian, "Modern Control Technology", 2nd Edition

Problems

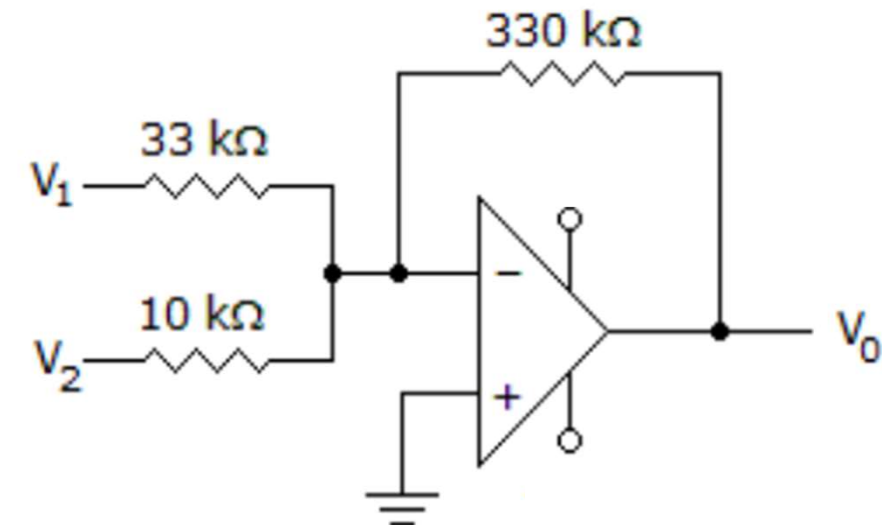1. Calculate the output voltage (V_o) if $V_1 = V_2 = 0.15V$




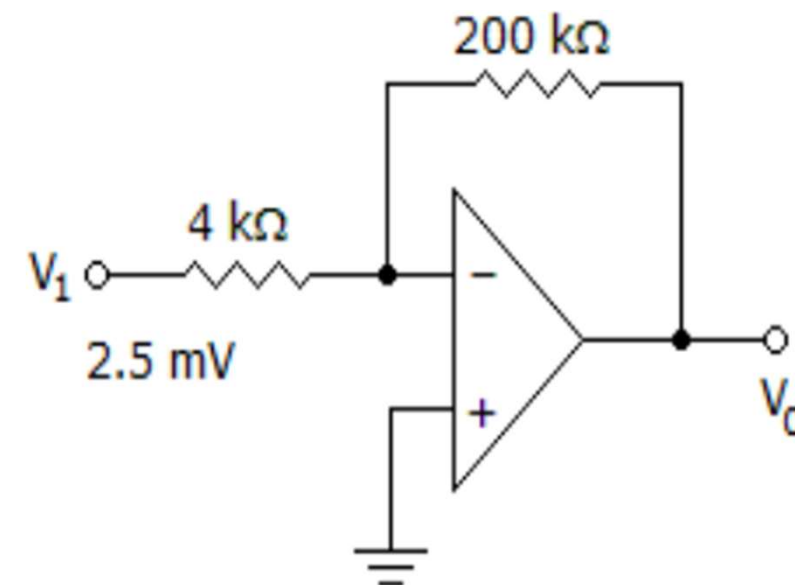2. Determine the output voltage (V_o) for this circuit with a sinusoidal input of 2.5 mV .




Problems

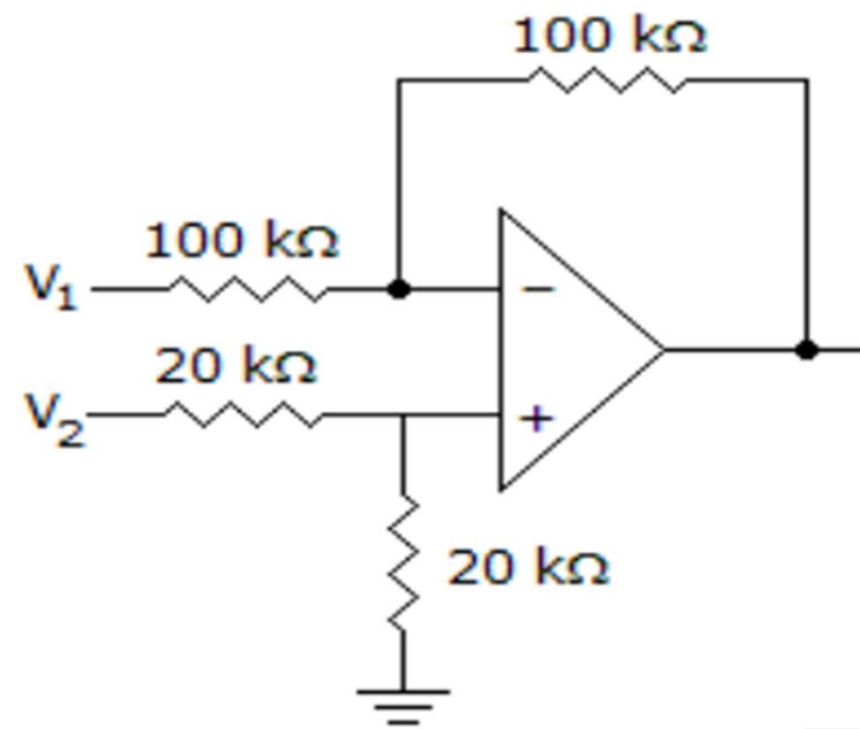3. Determine the output voltage (V_o) when $V_1 = V_2 = 1\text{ V}$



Problems

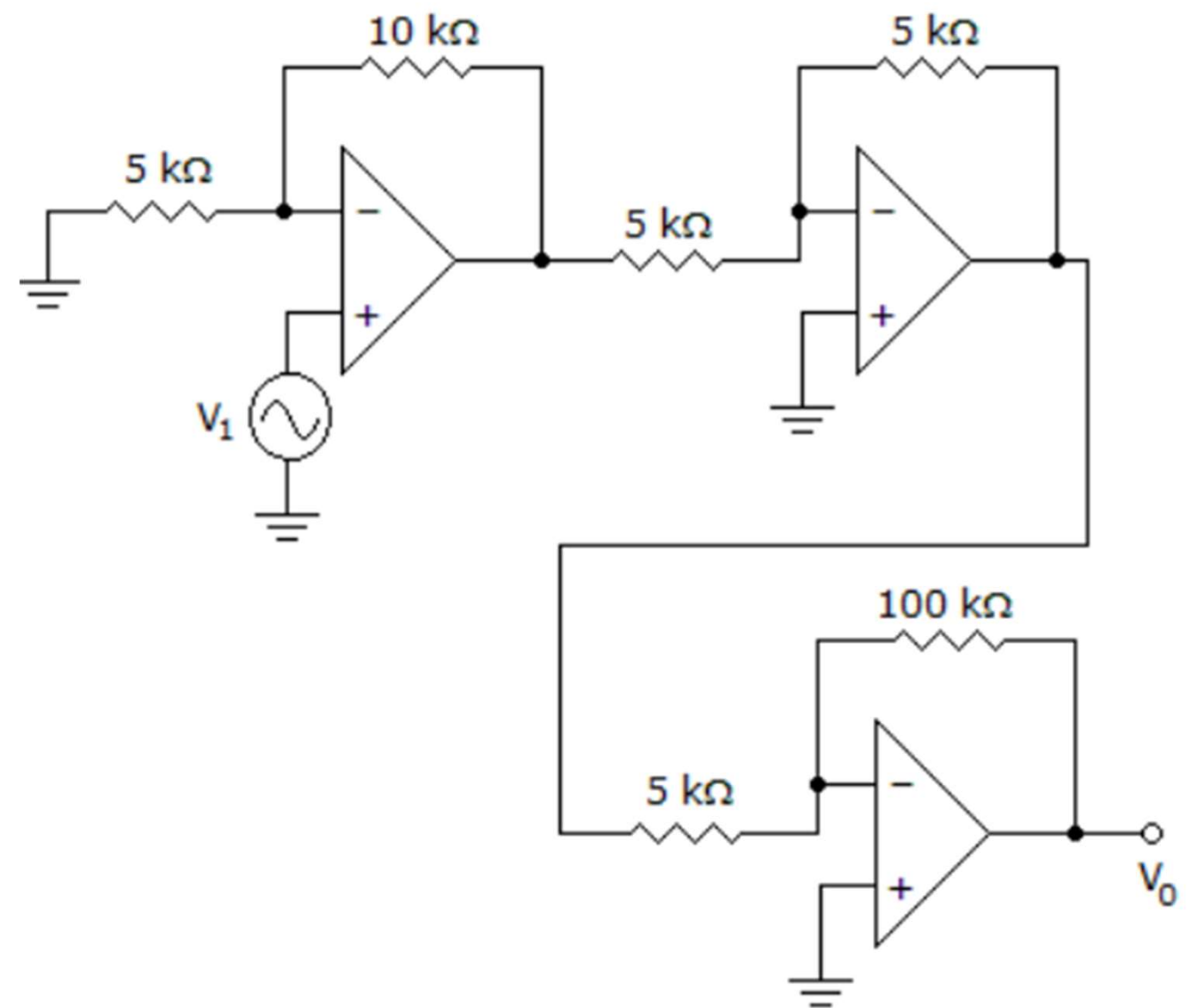4. Calculate the input voltage (V_1) if the final output (V_o) is 10.08 V



Reading

Introduction to Mechatronics and Measurement Systems, 4th Edition, *David G. Alciatore & Michael B. Hstand*

- *Chapter 5*

Thank you